

# COL215 Hardware Assignment 3

Arinjay Singhal 2023CS10041  
Vihaan Luhariwala 2023CS10151

November 2024

## 1 Introduction

The objective of the assignment is: implementation of AES decryption operation. The components involved are memory elements (RAM, ROM and registers), FSM and control unit.

## 2 Design

The design of the AES decryption operation is as follows:

- main control unit: it takes clk and reset as input and performs aes decryption on the input data from the memory.
- memory: it stores the input data, round keys and sbox values.
- main FSM: it controls the flow of the decryption operation.

## 3 Logic

We use memory elements to load the ciphertext, round keys, and the inverse S-box matrix. The ciphertext is processed through a series of steps: Add Round Key, Inverse Mix Columns, Inverse Shift Rows, and Inverse Sub Bytes, with each step controlled by an FSM. The final plaintext is then displayed on an FPGA board, one column at a time, using a segment display process. Each process has its own FSM, and an additional FSM manages transitions between these processes, all synchronized to a clock.

### 3.1 main control unit

It has following fsm's:

- cycle\_process : it updates the current fsm to the next fsm.
- whole\_state\_update : it updates the current 128 bit state by reading from the memory.
- main\_proc : it does the aes decryption operation on current 128 bit state.
- seg\_display : it displays the current 128 bit state.

## 3.2 memory

We generated 3 memories:

- sbox: it stores the sbox values.
- round\_keys: it stores the round keys.
- input: it stores the input data.

We used block memory generator from IP catalog to generate the memories. The width of memories is 8 bit and depth is 256 for sbox and 160 for round keys and 32 for input. We then load the memories with the COE files and fill empty spaces with 0.

 


Figure 1: Block diagram of memory

## 3.3 main FSM

Main fsm controls the flow of the decryption operation. It is divided into round\_counter, process\_counter, intermediate\_counter and step\_counter. The delay to switch between states is 10 clock cycles. Round\_counter is used to keep track of the current round (10 rounds in total). Process\_counter is used to keep track of the current process (4 processes of AES decryption). Intermediate\_counter tracks the current intermediate state (4 (in case of row operation) or 16 (in case of byte operation)). Step\_counter is used to keep track of the current step (depends on the process).

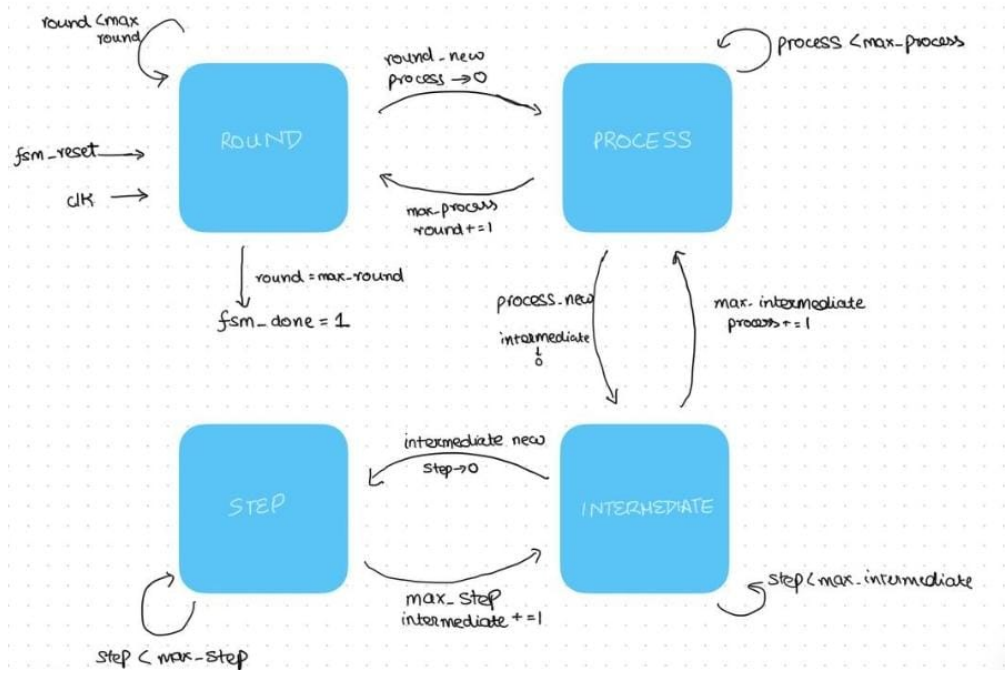


Figure 2: Block diagram of FSM

### 3.4 whole\_state\_update

It reads the 128 bit state from the memory and updates the current state signal (128 bit) with the read value. It has 2 steps indicating read and update. These have delay of 10 clock cycles.

 


Figure 3: Block diagram of whole\_state\_update

### 3.5 main\_proc

It performs the AES decryption operation on the current state. It takes its states from main FSM and performs the operations according to the signals.

### 3.6 seg\_display

It displays the current state on the 7 segment display. We define 4 output columns before calling this state. It switches between the columns after  $2^{28}$  clock cycles.

 


Figure 4: Block diagram of `seg_display`

### 3.7 cycle\_process

It updates the current fsm to the next fsm based on the done signal from the current fsm.

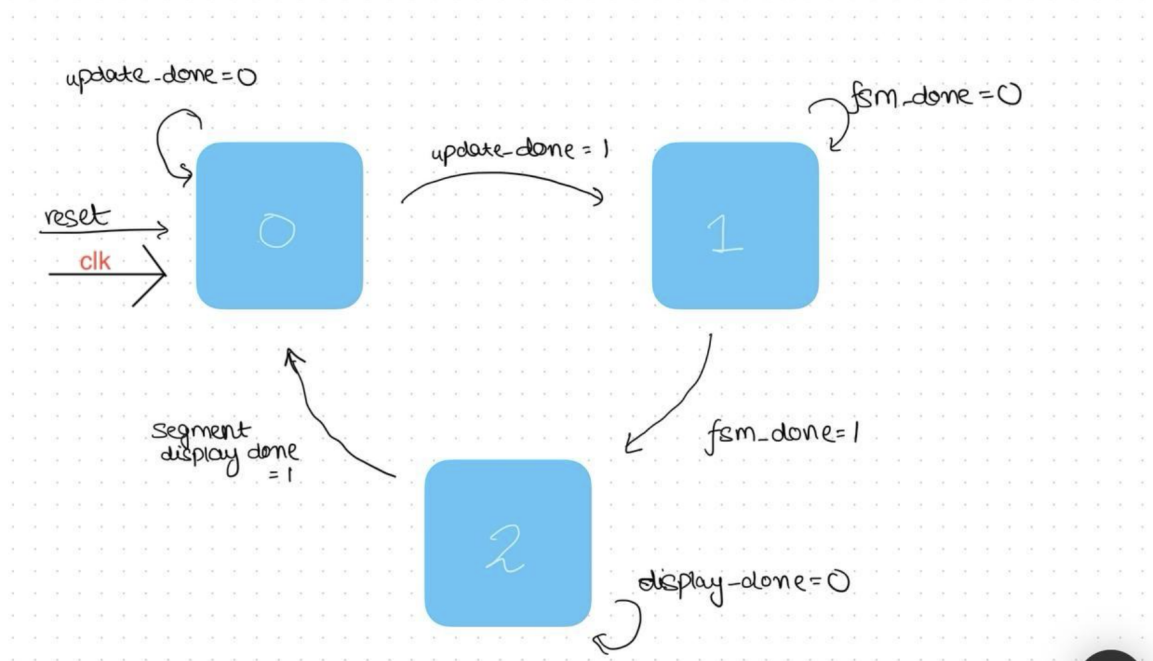


Figure 5: Block diagram of `cycle_process`



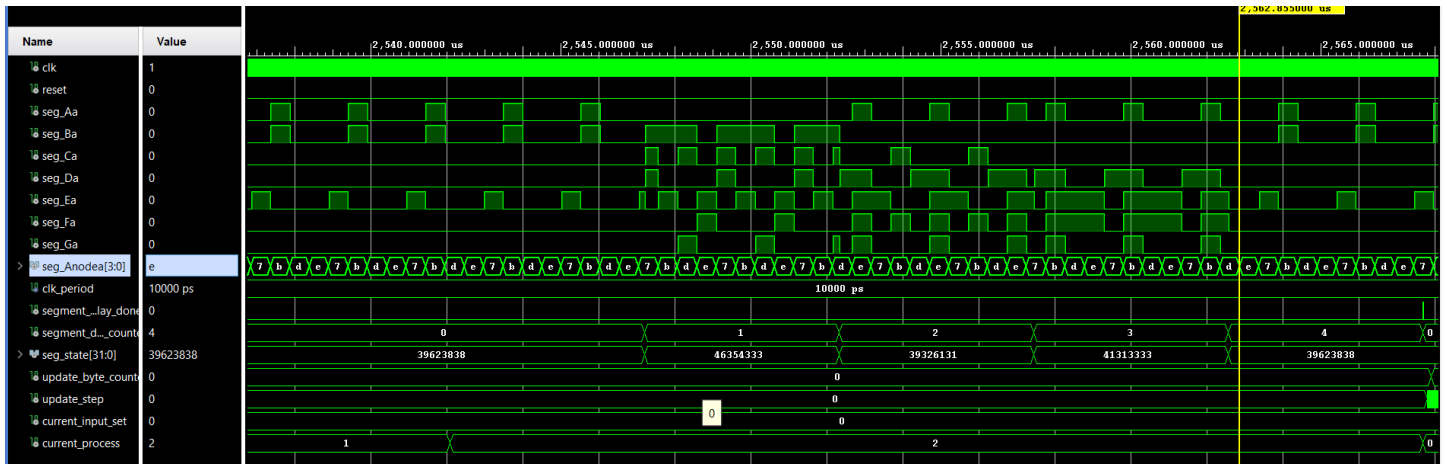


Figure 9: Simulation of main control unit

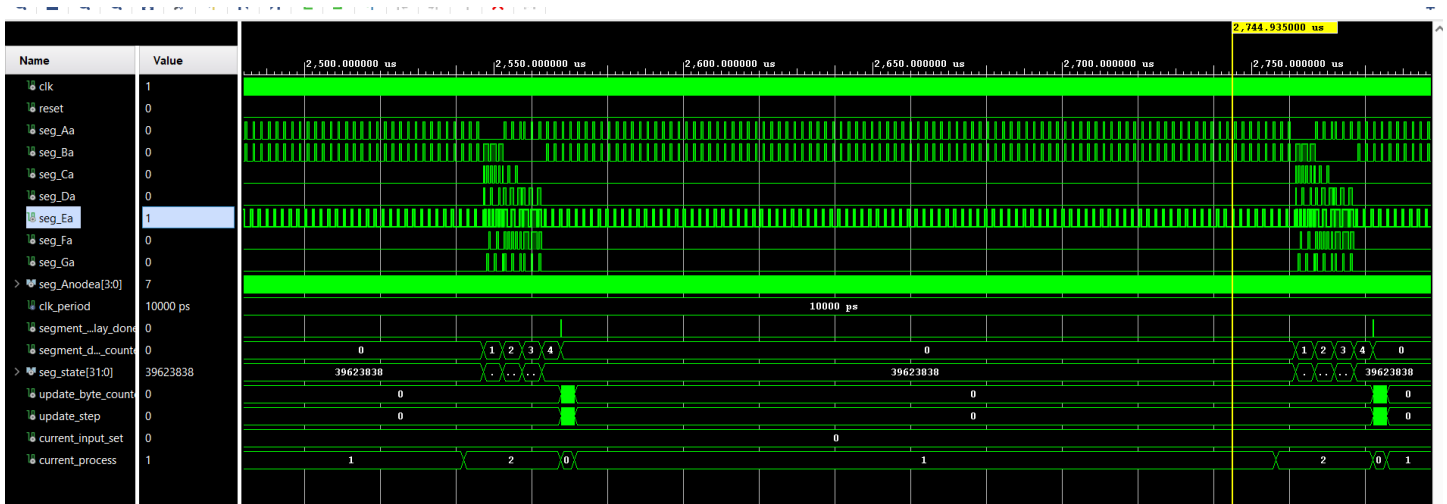


Figure 10: Simulation of main control unit

## 4.3 RTL Schematic

### 4.3.1 Main FSM

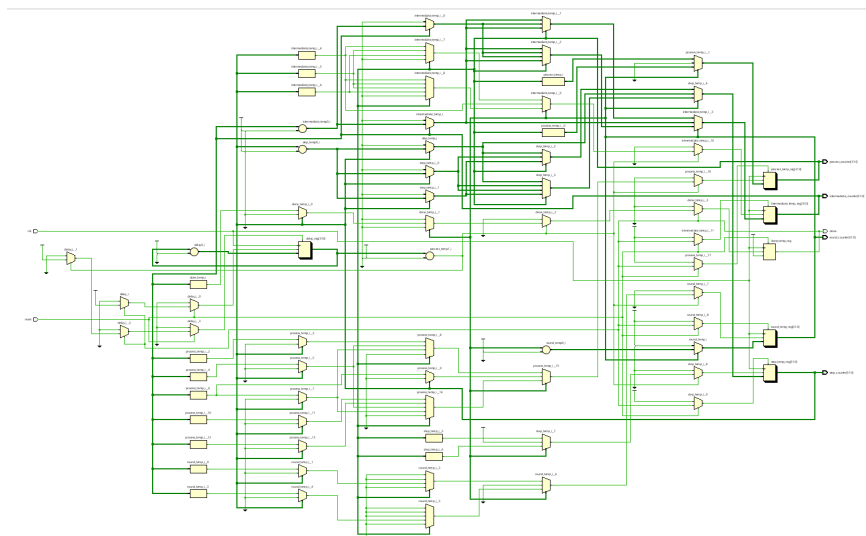


Figure 11: RTL Schematic

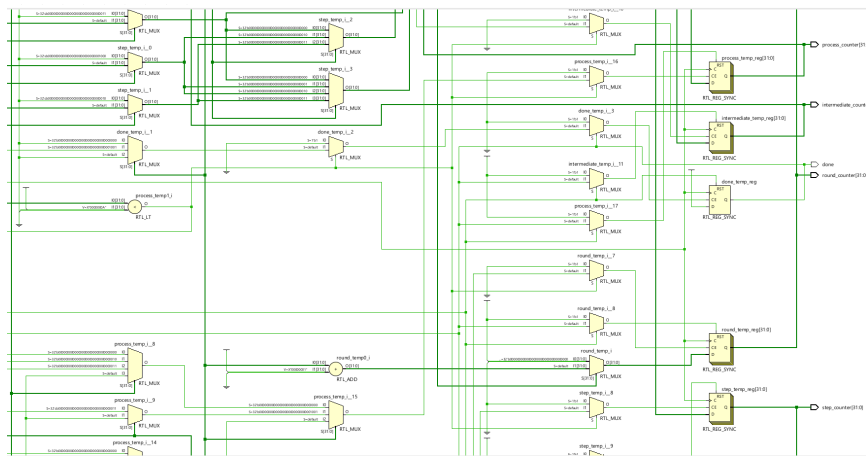


Figure 12: RTL Schematic

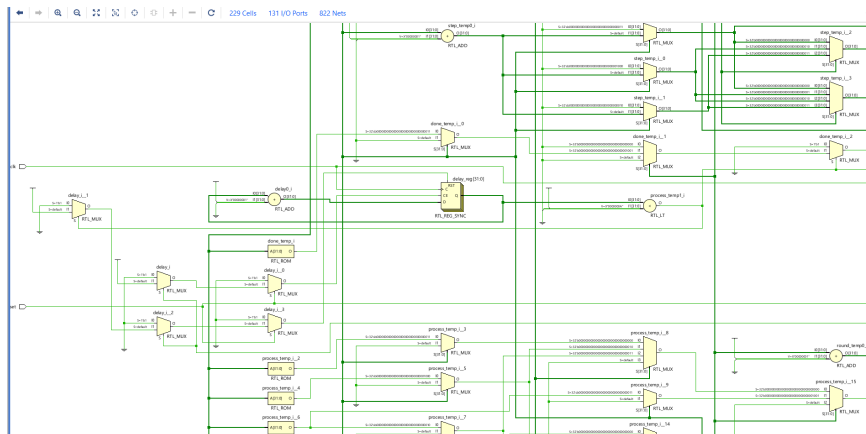


Figure 13: RTL Schematic

### 4.3.2 Main control unit

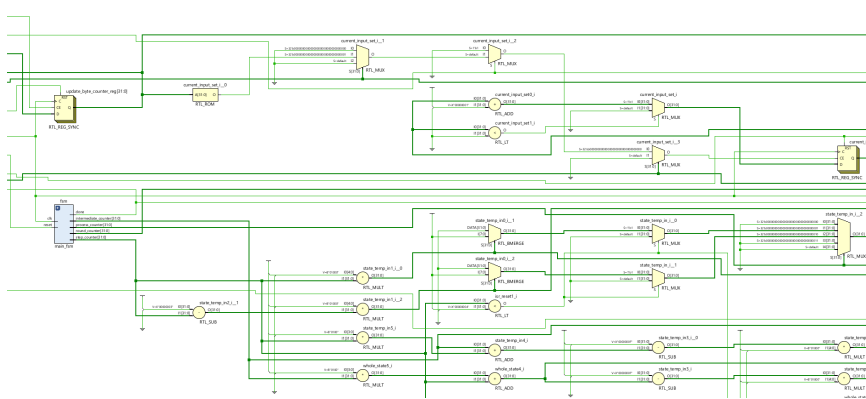


Figure 14: RTL Schematic

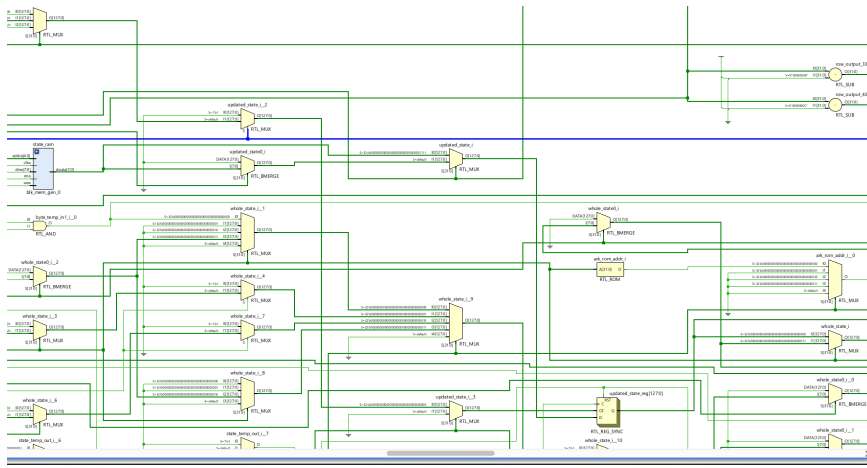


Figure 15: RTL Schematic

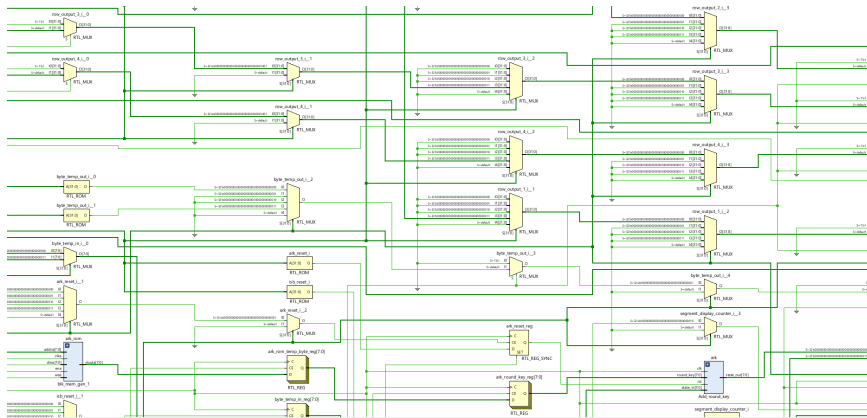


Figure 16: RTL Schematic

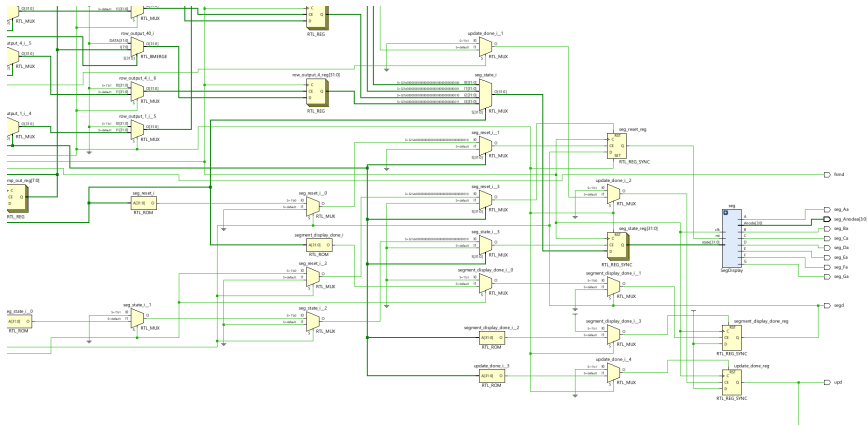


Figure 17: RTL Schematic



## 5 Synthesis Report

```
3 -----
4 Start RTL Component Statistics
5 -----
6 Detailed RTL Component Info :
7 +---Adders :
8     2 Input    32 Bit    Adders := 18
9     3 Input    32 Bit    Adders := 2
0     2 Input    28 Bit    Adders := 1
1     2 Input     2 Bit    Adders := 1
2 +---XORs :
3     2 Input     8 Bit    XORs := 18
4     9 Input     8 Bit    XORs := 2
5     8 Input     8 Bit    XORs := 2
6 +---Registers :
7             128 Bit    Registers := 2
8             32 Bit    Registers := 15
9             28 Bit    Registers := 1
0             8 Bit    Registers := 18
1             7 Bit    Registers := 1
2             5 Bit    Registers := 1
3             4 Bit    Registers := 3
4             2 Bit    Registers := 2
5             1 Bit    Registers := 20
6 +---Muxes :
7     2 Input    128 Bit    Muxes := 15
8     4 Input    128 Bit    Muxes := 5
9     4 Input    32 Bit    Muxes := 19
0     2 Input    32 Bit    Muxes := 45
1     6 Input    32 Bit    Muxes := 1
2     3 Input    32 Bit    Muxes := 2
3     2 Input     8 Bit    Muxes := 15
4     4 Input     8 Bit    Muxes := 2
5     2 Input     7 Bit    Muxes := 3
6     2 Input     5 Bit    Muxes := 2
7     4 Input     4 Bit    Muxes := 1
8     2 Input     1 Bit    Muxes := 62
9     4 Input     1 Bit    Muxes := 32
0     6 Input     1 Bit    Muxes := 3
1     3 Input     1 Bit    Muxes := 3
2 -----
3 Finished RTL Component Statistics
```

Figure 18: Synthesis Report

```
-----
Start Handling Custom Attributes
-----
Finished Handling Custom Attributes : Time (s): cpu = 00:00:25 ; elapsed = 00:00:30 . Memory (MB): peak = 1958.621 ; gain = 1030.129
-----
Finished RTL Optimization Phase 1 : Time (s): cpu = 00:00:25 ; elapsed = 00:00:30 . Memory (MB): peak = 1958.621 ; gain = 1030.129
-----
Netlist sorting complete. Time (s): cpu = 00:00:00 ; elapsed = 00:00:00.087 . Memory (MB): peak = 1958.621 ; gain = 0.000
INFO: [Netlist 29-17] Analyzing 3 Unisim elements for replacement
INFO: [Netlist 29-28] Unisim Transformation completed in 0 CPU seconds
INFO: [Project 1-570] Preparing netlist for logic optimization

Processing XDC Constraints
Initialising timing engine
Parsing XDC File [D:/basys3.xdc]
Finished Parsing XDC File [D:/basys3.xdc]
INFO: [Project 1-236] Implementation specific constraints were found while reading constraint file [D:/basys3.xdc]. These constraints will be ignored for synthesis but will be used in implementation. Imp
Resolution: To avoid this warning, move constraints listed in [.Xil/main_control_propImpl.xdc] to another XDC file and exclude this new file from synthesis with the used_in_synthesis property (File Propo
Parsing XDC File [D:/hw32/hw32.runs/synth_1/dont_touch.xdc]
Finished Parsing XDC File [D:/hw32/hw32.runs/synth_1/dont_touch.xdc]
Completed Processing XDC Constraints

Netlist sorting complete. Time (s): cpu = 00:00:00 ; elapsed = 00:00:00.001 . Memory (MB): peak = 1958.621 ; gain = 0.000
INFO: [Project 1-111] Unisim Transformation Summary:
No Unisim elements were transformed.

Constraint Validation Runtime : Time (s): cpu = 00:00:00 ; elapsed = 00:00:00.028 . Memory (MB): peak = 1958.621 ; gain = 0.000
INFO: [Designutils 20-5440] No compile time benefit to using incremental synthesis; A full resynthesis will be run
INFO: [Designutils 20-4379] Flow is switching to default flow due to incremental criteria not met. If you would like to alter this behaviour and have the flow terminate instead, please set the following
-----
Finished Constraint Validation : Time (s): cpu = 00:00:35 ; elapsed = 00:00:44 . Memory (MB): peak = 1958.621 ; gain = 1030.129
-----
Start Loading Part and Timing Information
-----
Loading part: xc7a35tcpg236-1
-----
Finished Loading Part and Timing Information : Time (s): cpu = 00:00:35 ; elapsed = 00:00:44 . Memory (MB): peak = 1958.621 ; gain = 1030.129
```

Figure 19: Synthesis Report

```

-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
|1| BUFG | 1|
|2| CARRY4 | 171|
|3| LUT1 | 230|
|4| LUT2 | 404|
|5| LUT3 | 93|
|6| LUT4 | 248|
|7| LUT5 | 299|
|8| LUT6 | 756|
|9| MUXF7 | 3|
|10| RAMB18E1 | 3|
|13| FDCE | 87|
|14| FDPE | 4|
|15| FDRE | 934|
|16| FDSE | 34|
|17| IBUF | 2|
|18| OBUF | 14|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:01:33 ; elapsed = 00:01:50 . Memory (MB): peak = 1958.621 ; gain = 1030.129
-----

```

Figure 20: Synthesis Report

## 6 Utilization Report

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	1777	0	0	20800	8.54
LUT as Logic	1777	0	0	20800	8.54
LUT as Memory	0	0	0	9600	0.00
Slice Registers	1059	0	0	41600	2.55
Register as Flip Flop	1059	0	0	41600	2.55
Register as Latch	0	0	0	41600	0.00
F7 Muxes	3	0	0	16300	0.02
F8 Muxes	0	0	0	8150	0.00

Figure 21: Utilization Report

Total	Clock Enable	Synchronous	Asynchronous
0	-	-	-
0	-	-	Set
0	-	-	Reset
0	-	Set	-
0	-	Reset	-
0	Yes	-	-
4	Yes	-	Set
87	Yes	-	Reset
34	Yes	Set	-
934	Yes	Reset	-

Figure 22: Utilization Report

Site Type	Used	Fixed	Prohibited	Available	Util%
Block RAM Tile	1.5	0	0	50	3.00
RAMB36/FIFO*	0	0	0	50	0.00
RAMB18	3	0	0	100	3.00
RAMB18E1 only	3				

Figure 23: Utilization Report

Site Type	Used	Fixed	Prohibited	Available	Util%
BUFGCTRL	1	0	0	32	3.13
BUFIO	0	0	0	20	0.00
MMCME2_ADV	0	0	0	5	0.00
PLLE2_ADV	0	0	0	5	0.00
BUFMRCE	0	0	0	10	0.00
BUFHCE	0	0	0	72	0.00
BUFR	0	0	0	20	0.00

Figure 24: Utilization Report

Site Type	Used	Fixed	Prohibited	Available	Util%
Bonded IOB	16	0	0	106	15.09
Bonded IPADs	0	0	0	10	0.00
Bonded OPADs	0	0	0	4	0.00
PHY_CONTROL	0	0	0	5	0.00
PHASER_REF	0	0	0	5	0.00
OUT_FIFO	0	0	0	20	0.00
IN_FIFO	0	0	0	20	0.00
IDELAYCTRL	0	0	0	5	0.00
IBUFDS	0	0	0	104	0.00
GTE2_CHANNEL	0	0	0	2	0.00
PHASER_OUT/PHASER_OUT_PHY	0	0	0	20	0.00
PHASER_IN/PHASER_IN_PHY	0	0	0	20	0.00
IDELAYE2/IDELAYE2_FINEDELAY	0	0	0	250	0.00
IBUFDS_GTE2	0	0	0	2	0.00
ILOGIC	0	0	0	106	0.00
OLOGIC	0	0	0	106	0.00

Figure 25: Utilization Report

Site Type	Used	Fixed	Prohibited	Available	Util%
BSCANE2	0	0	0	4	0.00
CAPTUREE2	0	0	0	1	0.00
DNA_PORT	0	0	0	1	0.00
EFUSE_USR	0	0	0	1	0.00
FRAME_ECCE2	0	0	0	1	0.00
ICAPE2	0	0	0	2	0.00
PCIE_2_1	0	0	0	1	0.00
STARTUPE2	0	0	0	1	0.00
XADC	0	0	0	1	0.00

Figure 26: Utilization Report

Ref Name	Used	Functional Category
FDRE	934	Flop & Latch
LUT6	756	LUT
LUT2	404	LUT
LUT5	299	LUT
LUT4	248	LUT
LUT1	230	LUT
CARRY4	171	CarryLogic
LUT3	93	LUT
FDCE	87	Flop & Latch
FDSE	34	Flop & Latch
OBUF	14	IO
FDPE	4	Flop & Latch
RAMB18E1	3	Block Memory
MUXF7	3	MuxFx
IBUF	2	IO
BUFG	1	Clock

Figure 27: Utilization Report

## 7 Final result

We ran our module on the FPGA after loading the memories with the 128 bit COE file from moodle. The output was as expected and the 7 segment display showed the correct output.

 


Figure 28: output column 1 : F5C3



 


Figure 29: output column 2 : 92A1

 


Figure 30: output column 3 : A133

 


Figure 31: output column 4 : 9b88